

Announcements 3/18/10

Friday afternoon problem/question session: 3:30 – 5 at my office

Tonight's problem session:

7:30-8 review of circular motion and cross products, followed by homework.

SAs available for those who prefer to work on homework.

Reading:

Today: 26.1-2 (though probably we won't get to it)

Tuesday: 26.3-4

J.J. 3/18/2010

Last time: saw that as a capacitor discharges, at first it discharges rapidly (high current), and then as it continues, it slows down (less current).

Why? V_{cap} drives the current; as $V_{cap} = \frac{Q(t)}{C}$ decreases, so does the amount of current and thus how fast the cap discharges

Loop rule:

$$V_{cap}^{(t)} - I^{(t)}R = 0 \Rightarrow V_{cap}^{(t)} = I^{(t)}R \Rightarrow I(t) = \frac{V_{cap}(t)}{R}$$

Use $V_{cap}(t) = \frac{Q(t)}{C} \Rightarrow \cancel{Q(t)} = I^{(t)}R \Rightarrow I(t) = \frac{Q(t)}{RC}$

~~greatest current happens when charge is greatest.~~

Define $t=0$ as the time when first close switch;

at $t=0$, ~~initially~~ $Q(t=0) = Q_0$


$$\Rightarrow I(t=0) = \frac{V_{cap}(t=0)}{R} = \frac{Q_0/C}{R} = \frac{Q_0}{RC}$$

How does the current change with time?

To find this, use loop rule w/idea we had @ very end:

positive current comes from losing charge from \oplus cap plate

$$\Rightarrow I(t) = -\frac{dQ}{dt}$$

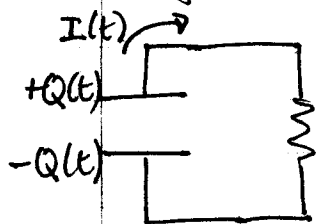


Substitute this into loop rule \Rightarrow "differential equation" for Q : ~~initially~~ $Q(t) = -\frac{dQ}{dt} RC$

Result of integrating this (and using initial conditions properly for limits) is an exponential decay:

$$Q(t) = Q_0 e^{-t/RC} \quad \text{and so} \quad I(t) = \frac{Q_0}{RC} e^{-t/RC}$$

~~initially~~

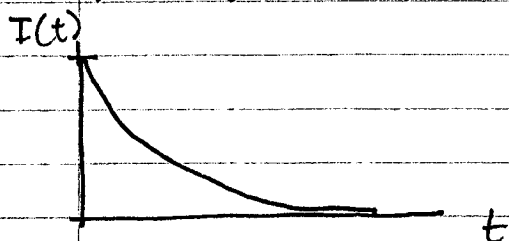What does this mean? Let's look at a graph:



max value at $t=0$

decreases rapidly at first, more slowly afterward

The product RC determines how quickly it decreases:

After a time $t=RC$, $I(t)$ and $Q(t)$ have dropped to $\frac{1}{e}$ times their initial values

$$I(t=RC) = I_0 e^{-RC/RC} = I_0 e^{-1} = \frac{I_0}{e}$$

$\frac{1}{e} \approx 0.37$ so rule of thumb is that after $t=RC$, current/charge has dropped ~~to 37%~~ to $\frac{1}{e}$ of its initial value

If you want to discharge fast need small RC

If you want to store lots of energy in the capacitor, need big C

\Rightarrow want small R to discharge a lot of energy rapidly!

Also initial current $= V_0/R$ determined entirely by R, V_0

Defibrillator: $100 \mu F$ cap, ~~what is the current~~

Resistance ^{ivity} of human body: very high ~~resistance~~


when dry — so need to bring resistance down to get rapid discharge

any EMT's in class?

Remember resistance $R = \frac{\rho L}{A}$ so make paddles on defib large

(Note to self: initial current $= \frac{Q_0}{RC}$ just as if

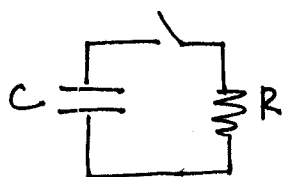resistor was driven by battery w/ $\mathcal{E} = Q_0/C$)



Sample problem

Goal: times it takes to reach various voltages

Principle: exponential decay of charge on capacitor \Rightarrow exp decay of V_{cap} too

$$V_{cap}(t) = \frac{Q(t)}{C} = \frac{Q_0}{C} e^{-t/RC} = V_0 e^{-t/RC}$$

(a) $V_{cap} = 3.7 \text{ V}$

Could recognize ~~this~~ as the 37% rule of thumb from before: V_{cap} has dropped to 37% of its initial value of 10 V.

Do it explicitly:

$$3.7 \text{ V} = 10.0 \text{ V} e^{-t/(10\Omega)(1.0 \text{ F})}$$

Need t : divide both sides by 10 V

$$\left(\frac{3.7 \text{ V}}{10.0 \text{ V}} \right) = e^{-t/10\text{s}}$$

Take \ln of both sides:

$$\ln(0.37) = \ln(e^{-t/10\text{s}}) = -\frac{t}{10\text{s}}$$

$$\ln(0.37) = -1 \Rightarrow -1 = -\frac{t}{10\text{s}}$$

$$10\text{s} = t$$

note $1\Omega \cdot 1\text{F} = 1\text{s}$

which you'll show on HW

$$1\Omega = 1\text{V}/1\text{A} \quad 1\text{F} = 1\text{C}/1\text{V}$$

(b) $V_{cap} = 0 \text{ V}$ amounts to asking: does the decay ever get all the way to zero? Do we ever have $e^{-t/RC} = 0$?

Not exactly... graph shows function never quite gets to zero.

Instead ask what is good enough?

$$\text{Then } 1.0 \times 10^{-2} \text{ V} = 10 \text{ V} e^{-t/RC}$$

$$1.0 \times 10^{-3} = e^{-t/RC}$$

$$\ln(1.0 \times 10^{-3}) = \ln(e^{-t/RC})$$

$$-6.9 = -\frac{t}{RC} \Rightarrow t = 6.9RC = 69 \text{ s}$$

$$V_{cap} = \frac{0.01}{10} \text{ V} = 0.001 \text{ V} \quad (0.01\% \text{ of original})$$

A capacitor with a capacitance of 1 F is charged to 10 V and then allowed to discharge through a 10 Ω resistor. How long does it take for the capacitor voltage to reach ~~0~~^{3.7} V? How long does it take for the capacitor to discharge completely?



initial $V_{cap} = 10$ V, then decreases

Need time $t = RC$ for Voltage to fall to 37% of its initial value

$$V_{cap}(t) = \frac{Q(t)}{C} = \frac{Q_0 e^{-t/RC}}{C} = V_0 e^{-t/RC}$$

Want t :

$$\ln\left(\frac{V_{cap}(t)}{V_0}\right) = \ln\left(e^{-t/RC}\right)$$

$$\ln\left(\frac{V_{cap}(t)}{V_0}\right) = -\frac{t}{RC}$$

$$\ln\left(\frac{3.7 \text{ V}}{10 \text{ V}}\right) = -\frac{t}{(10 \Omega)(1.0 \text{ F})}$$

$$-1 = -\frac{t}{10 \text{ s}}$$

$$10 \text{ s} = t$$

~~$$V = IR = 7$$~~


$$(1 \Omega)(1 \text{ F}) = 1 \text{ s}$$

~~$$V = IR \Rightarrow 1 \text{ V} = (1 \text{ A})(1 \Omega)$$~~

~~$$Q = CV \Rightarrow 1 \text{ C} = (1 \text{ F})(1 \text{ V})$$~~

When is $V_{cap} = 0$? Only when $e^{-t/RC} = 0$

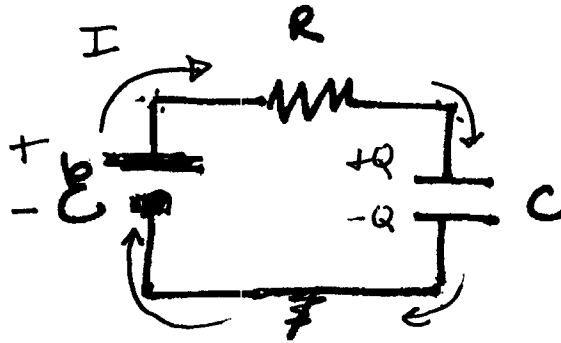A circuit consists of a battery with emf \mathcal{E} in series with a capacitor and a resistor. The switch is initially open and the capacitor is not charged. Then the switch is closed. How do the voltage across the capacitor V_{cap} and the current in the resistor I_R change as time goes on?



just as with
resistor ckts
at every instant,
 I is same all
around circuit

1. V_{cap} will increase and I_R will increase.

2. V_{cap} will increase and I_R will decrease.

3. V_{cap} will decrease and I_R will increase.


4. V_{cap} will decrease and I_R will decrease.

amount of I
changes in time
BUT same all
around @ any inst

$$\mathcal{E} - I(t)R - V_{\text{cap}}(t) = 0$$

$$\frac{\mathcal{E} - V_{\text{cap}}(t)}{R} = I(t)$$

11:50

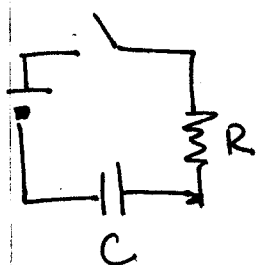long
conservative
hereWhat about charging?

Capacitor is initially uncharged, then close switch
 \boxed{CT} $V_{cap} \uparrow, I \downarrow$ ~~by course~~

Why?

Loop rule again!

$$\mathcal{E} - I(t)R - V_{cap}(t) = 0$$

(why do we subtract $V_{cap}(t)$? current will charge the plate next to \oplus terminal \oplus , so crossing V_{cap} from \oplus to \ominus — losing potential)

V_{cap} increases: we know we start at $V_{cap}(t=0) = 0$ b/c unchanged

eventually reach maximum value (what? \mathcal{E})
 when fully charged (no more current flows)

As V_{cap} increases, $I(t)R$ decreases so as to keep loop rule true


Initial value of $I(t=0)$? $I(t=0) = \frac{\mathcal{E}}{R}$ b/c $V_{cap}(t=0) = 0$

Final value of I ? Zero

In fact expect exactly same $I(t)$ as discharging:

initially \mathcal{E} drives current

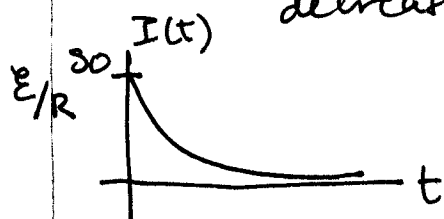
as V_{cap} increases, $\mathcal{E} - V_{cap}(t)$ is driving current \rightarrow decreasing!



and thus

$V_{cap}(t)$ must
 be $\mathcal{E} - I(t)R$

so just same shape flipped over

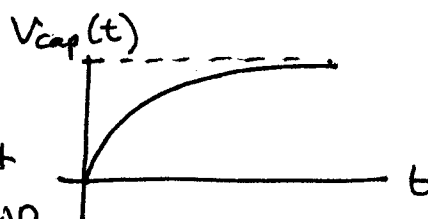

Mathematically: follow similar procedure of using relationship between Q & I in loop rule, but now current is adding charge to capacitor

$$\Rightarrow I(t) = \frac{dQ}{dt}$$

Turns out to be easier to find $I(t)$ first

$$\rightarrow I(t) = I_0 e^{-t/RC} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

same! and same time constant

$$\text{Then } V_{\text{cap}}(t) = \mathcal{E} - I(t)R = \mathcal{E}(1 - e^{-t/RC})$$

same time const, incr.


$$Q(t) = CV_{\text{cap}}(t) = C\mathcal{E}(1 - e^{-t/RC})$$

Use this equation the same way as the other one, so problems are very similar

This time rule of thumb gives us at $t = RC$, current is 37% of initial current, but voltage is $(1 - e^{-1})\mathcal{E} \approx (1 - 0.37)\mathcal{E} = 0.63\mathcal{E}$

Two time constants: $t = 2RC \Rightarrow (1 - e^{-2})\mathcal{E} \approx 0.86\mathcal{E}$
slows down!


Does it matter if instead we have

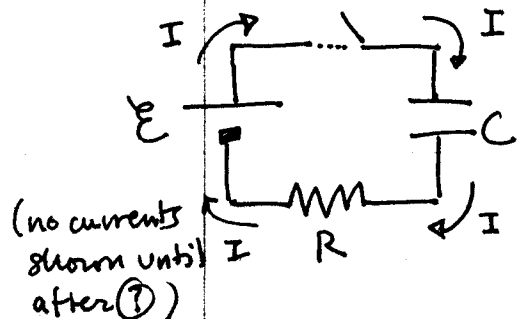

No! Current is same everywhere around ckt once switch is closed. Varies in time, but at any instant have same current throughout.

(Note: switch is also like a capacitor but with negligibly small capacitance, so current flows only for briefest instant in open ckt config)

What about more complex circuits?

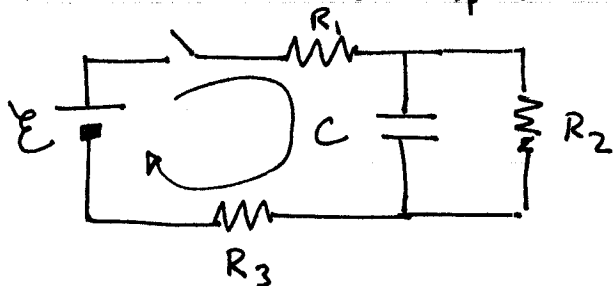

When first close switch, capacitor is uncharged
 $\rightarrow V_C = 0 \rightarrow$ it behaves like a short circuit
 and all current travels down its branch
 (C and R_2 are in parallel
 if $V_C = 0$ must also have $V_{R_2} = 0$
 this can only happen if $I_{R_2} = 0$)

How much current is drawn from battery initially?
 Loop rule for left loop:

$$\mathcal{E} - I_{\text{batt}} R_1 - I_{\text{batt}} R_3 = 0 \quad \begin{matrix} V_{\text{cap}} = 0 \\ V_{R_2} = 0 \end{matrix}$$

$$\Rightarrow I_{\text{batt}} = \frac{\mathcal{E}}{R_1 + R_3}$$

How fast does it charge?

Complicated: but at initial instant, like $R = R_1 + R_3$
 $\Rightarrow \tau = RC = (R_1 + R_3)C$

After a very long time, C is fully charged

What is its final voltage? $V_{\text{cap}} < \mathcal{E}$ b/c current still goes around outer loop

Must have $V_{\text{cap}} = V_{R_2}$ so must be a current there!


~~no current goes down C~~ no current goes down C ("open circuit")
 Once fully charged, \Rightarrow current only around outer loop

Find that current, use it to find $V_{R_2} \Rightarrow V_{\text{cap}}$

$$\mathcal{E} - I R_1 - I R_2 - I R_3 = 0 \Rightarrow I = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$


$$V_{R_2} = I R_2 = \mathcal{E} R_2 / (R_1 + R_2 + R_3)$$

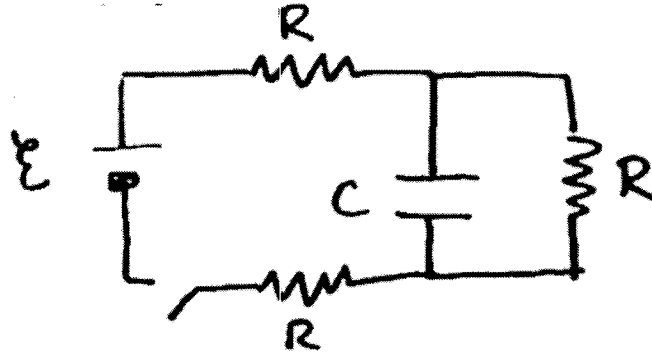In the circuit shown, the capacitor is initially uncharged. Immediately after the switch is closed, what is the voltage across the capacitor, V_C ?



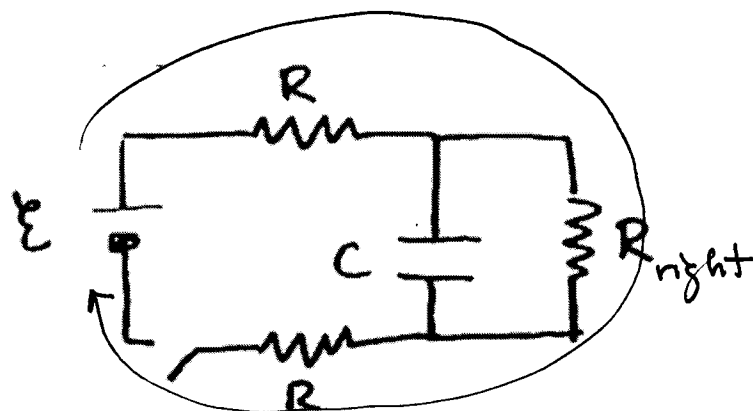1. $V_C = \mathcal{E}$
2. $V_C = \mathcal{E}/2$
3. $V_C = \mathcal{E}/3$
4. $V_C = \mathcal{E}/4$
5. $V_C < \mathcal{E}$ but not sure how much less.
6. $V_C = 0$.

In the circuit shown, a long time after the switch is closed, what is the voltage across the capacitor, V_C ?



1. $V_C = \mathcal{E}$

2. $V_C = \mathcal{E}/2$

3. $V_C = \mathcal{E}/3$

4. $V_C = \mathcal{E}/4$

→ 5. $V_C < \mathcal{E}$ but not sure how much less.

6. $V_C = 0$.

C is "open circuit"
at this point
(when fully charged)

No current in C branch
Current only flows around
outside loop

V_{cap} must equal $V_{R_{right}}$

$$\left. \begin{array}{l} V_{top} = IR \\ V_{right} = IR \\ V_{bottom} = IR \end{array} \right\} \mathcal{E} - 3IR = 0$$

$$\Rightarrow I = \frac{\mathcal{E}}{3R}$$

$$V = \frac{\mathcal{E}}{3} \text{ for any resistor}$$